

The μ Current

A professional precision current adapter for Multimeters

By David L. Jones

(david@alternatezone.com)

www.alternatezone.com/electronics/ucurrent

www.eevblog.com

(Copyright© 2010 David L. Jones – Freely distributable in the original unaltered PDF format ONLY)



A current adapter for multimeters?

“But don’t most multimeters already have current measurement ranges?” I hear you ask.

Well, yes, they do of course. But most multimeters, be they a no-name \$10 hardware store throw-away model, or a \$1000 highly accurate brand name meter, all suffer from two rather annoying issues with their current measurement ranges - burden voltage and reduced accuracy.

Burden Voltage

The biggest problem with current measurement ranges is called “burden voltage”. This is the voltage that the internal current shunt resistor drops as you pass your circuit current through it.

The burden voltage is typically specified in millivolts per Amps (mV/A). The value will change for different current ranges, so you might have 1mV/A, 1mV/mA, or 1mV/μA for example.

Normally you may not give burden voltage a second thought, as like many, you probably think it’s fairly insignificant in most applications. In fact, most people would be hard pressed to tell you what the burden voltage of their particular multimeter actually is. It’s usually buried away in the user manual, if it’s mentioned at all. Next time you borrow a colleague’s meter, ask them what the burden voltage is, and watch their reaction...

At small displayed currents the burden voltage is usually not an issue, but at larger displayed currents (relative to Full-Scale) the burden voltage can be very high, even in the order of several volts! This can often force you to use a higher current range (with a lower current shunt resistor), with subsequent loss of resolution and (often) accuracy.

You may have encountered this many times before as your circuit either not working or “playing up” on too low a current range – that’s the burden voltage at work, starving your circuit of the voltage it needs to function correctly. You usually have no option but to reluctantly switch to a higher current range to lessen the effect.

The problem can also be highlighted with the many 4 ½ digit or “10000 count” meters on the market. In theory they allow you to get an extra digit of resolution over a 3½ digit meter. But you may now find yourself trying to measure for example 990.0µA on the 1mA range with a burden voltage of just under 1V. Can your circuit really handle a 1V drop?

The burden voltage of a multimeter is determined primarily by the shunt resistor used for measurement, but on the higher current ranges (mA & A) it also includes the protection fuse resistance, and to a much lesser extent, any switch and test lead contact resistance. Some manufacturers will specify it as a total, or just the shunt resistor, or in many cases not mention it at all!

Some meters will specify it as a maximum voltage drop only. For example, “300mV max”. In this case, to get the mV/A value you simply divide that voltage by the full-scale range current.

Low Voltage Current Measurement

The recent trend toward low voltage microcontrollers and other silicon devices (some operating as low as 1V or less!) have really highlighted the need for consideration of the burden voltage when measuring the chip current from its supply rail. 3.3V supplies have been entrenched everywhere for a long time now, and the trend is going lower.

A common task these days is to measure the accurate sleep and operating current of a microcontroller for instance. Indeed, with the lower the supply voltage of today’s battery powered circuits, the greater the requirement to more accurately measure the supply current. So the industry has changed, but meters haven’t really kept up with the pace when it comes to accurate current measurement. You think they may have as meters are getting more “accurate” for less cost, but that’s only part of the story.

Let’s look at how the supply voltage can impact your current measurement, or vice-versa as the case may be:

Lets say you want to measure the supply current of a chip or circuit taking 200mA using say a 4000 count meter on the 400mA range. A not uncommon scenario, and one you would think would be pretty easy for any mutlimeter to handle right? – Hold on...

A typical high end “accurate” multimeter will have a “low” 1mV/mA burden voltage (about as low as it gets), so this means the meter will drop 200mV across its shunt resistor at 200mA. This represents an almost tolerable 4% ($200\text{mV} / 5\text{V} * 100$) of a 5V supply voltage. This may not be a big deal if your supply voltage is spot on 5V, as your chip will get 4.8V and still be within spec. But what if it’s already say 4.8V?, your chip or circuit is now getting 4.6V and may be outside of its operational spec. This already shows the limitation of the current range on a typically mid to high end multimeter. Not to even mention the circuit current can differ when you lower the rail by 0.2V...

Let's now say you need to do the same thing on a modern circuit or chip with say a 1.2V power supply. That same 200mV burden voltage is now a whopping 17% ($200\text{mV} / 1.2\text{V} * 100$) of the supply voltage. Your circuit will likely fail to function correctly and this is clearly not acceptable, not to mention inaccurate.

Think this is only a problem with "cheap" meters? Think again. The Fluke 87-V, probably the most popular high-performance meter available has a burden voltage of 1.8mV/mA (which is still pretty good). So the above numbers are even worse – a 360mV drop for a 200mA current.

Sure, you can switch up a current range, using the 10A jack, with its burden voltage of say 10mV/A, giving you a very nice drop of only 2mV. But your display is now showing 0.200 or 0.20 instead of 200.0 – you've just lost a valuable digit or two of resolution. And the higher 10A current range is likely much less accurate than the mA range too!

Let's have a look at the quoted burden voltage of some typical multimeters:

Multimeter Model	Approx Cost(\$)	Burden Voltage (mA range)	Burden Voltage (μA range)
Meterman 5XP (3.5 digit)	\$65	1V max	300mV max
JayTech QM-1340 (4.5 digit)	\$99	5mV/mA	0.11mV / μA
Meterman 30XR	\$120	4.6mV / mA	1mV / μA
Protek 506	\$175	1mV / mA	1mV / μA
Meterman 37XR (10,000 count)	\$250	10mV / mA	1mV / μA
B&K 390A (4000 count)	\$380	2V max	500mV max
Fluke 77 series III (3.5 digit)	\$400	6 mV / mA	N/A
Fluke 77 series IV (6000 count)	\$425	2mV / mA	N/A
Fluke 79 series III (3.5 digit)	\$375	11mV / mA	N/A
Fluke 177/179 series IV (6000 count)	\$430	2mV / mA	N/A
Fluke 27	\$900	5.6mV / mA	0.5mV / μA
Fluke 80 series V (4.5 digit)	\$720	1.8mV / mA	0.1mV / μA
Agilent U1251A (4.5 digit)	\$680	1mV / mA	0.1mV / μA
Extech MM570 (500,000 count)	\$680	3.3mV / mA	0.15mV / μA
Fluke 289 (50,000 count)	\$950	1.8mV / mA	0.1mV / μA
Gossen MetraHit E-XTRA (60,000 count)	\$1700	300mV max	150mV max
Fluke 8808A (5.5 digit)	\$1100	1mV / mA	1mV max
Fluke 8846A (6.5 digit)	\$2100	500mV max	15mV max
Keithley 197A Microvolt (5.5 digit)	N/A	300mV max	300mV max

As you can see from the table, things can improve a bit with the more expensive meters, particularly on the μA ranges. But an expensive precision meter is by no means a guarantee of a low burden voltage. Even many very expensive top-of-the-line bench meters can have unacceptable burden voltages for many applications.

It should be noted that whilst some meters will have a fixed burden voltage for all mA ranges, others like the Meterman 30XR have individual specs for each range – in this case: 2mA range = 100mV/mA, 20mA = 13mV/mA, and 200mA = 4.6mV/mA

Some popular and highly regarded meters like the Meterman 37XR and Fluke 79 are particularly bad on their mA range, an order of magnitude worse than some cheaper meters – beware.

Take the above example again, the Meterman 37XR would drop a whopping 2V ($10\text{mV} \times 200$) on its mA range for 200mA. Not much good when your supply voltage is only 3.3V, or 5V, or even 12V.

And the 37XR is a relatively expensive 10000 count meter that is supposed to be capable of measuring 999.9mA on its 1A range – which it will try to do. But that would be a gigantic 10V drop which the meter itself cannot even handle, so it's limited to a nominal 400mA with a 4V drop on that range. Crazy huh?

I'm sure by now you are getting the idea that burden voltage can be a real hidden problem lurking in your meter. What is *your* meter rated at?

Accuracy

And the second problem mentioned? That would be one of accuracy. Most multimeters will have a much wider accuracy specification for current than they will for the DC voltage ranges, or the "Basic DC accuracy" as it's called.

The Meterman 37XR for example is quite an accurate meter at 0.1%(+5 counts) on DC volts, and is sold and marketed as such. But its current accuracy?, a not so impressive 0.5%(+10 counts) on DC current, jumping to 1.5% for the 10A range.

An even better example is the Fluke 27, with 0.1%(+1 counts) DC volts accuracy and 0.75%(+2 counts) mA/uA DC current accuracy.

Most other meters are very similar, with a factor of 5 or more between the DC volts and DC current accuracy being quite typical.

This issue is more prevalent with DC than AC, but can also apply to the AC voltage vs AC current ranges as well. Some meters can actually have very poor AC current accuracy and/or reduced AC frequency response compared to their AC millivolt range. Take the Fluke 27 again as an example. The ACV accuracy is 0.5%+3 to 2KHz, but the AC current ranges are only 1.5%+2 to 1KHz.

The Solution

You guessed it, the project to be presented here presents a neat solution to these issues. The μ Current (pronounced "micro current") is a simple yet accurate professional grade precision amplified current adapter for multimeters. It provides in many cases up to a 100 fold reduction in burden voltage for a given current range!

An additional feature is a nA current range not found on most multimeters at any price. This gives any cheap 3.5 digit multimeter the ability to resolve 0.1nA (100pA), and 0.01nA (10pA) on a 4.5 digit multimeter. All with an excellent accuracy of <0.2%.

The μ Current is in many cases also able to improve upon your meters current range accuracy by using your meters more accurate mVDC or mVAC voltage ranges instead to display the DC or AC current. With AC the frequency response extends flat up to 10KHz, but THD increases substantially above 2KHz. Still a very respectable AC response range, surpassing that of many meters on current and voltage ranges.

Typical accuracy of the μ Current itself is better than 0.2% on the μ A and nA ranges, and 0.5% or better on the mA range. Unfortunately it is not easy to obtain a 0.1% precision shunt resistor for the mA range, as the 10 milliohm value is too low.

The burden voltage of the μ Current is a fixed $10\mu\text{V}/\mu\text{A}$ and $10\mu\text{V}/\text{nA}$ on the lower ranges, and varies on the mA range due to the switch resistance, but $70\mu\text{V}/\text{mA}$ is a nominal upper figure. These figures are unmatched by almost any meter on the market.

So for example at a full scale of say $1000\mu\text{A}$, that's a maximum burden voltage of only 10mV. So measuring the current rail of a 1.2V logic supply with full scale resolution would give you a worst case drop of around 0.8%, a fairly insignificant figure.

The output voltage in mV is directly proportional to the input current, so you can simply read the current value from your multimeter's mV DC range.

The μ Current thus effectively eliminates any issues to do with burden voltage by making it insignificant in all but the most extreme applications.

How It Works

A current adapter is basically just a shunt resistor with an amplifier, and that is essentially all the μ Current is. But there are a few extra neat features to the design to make it as professional and handy as possible, as we'll see.


The heart of the design is U1, a Maxim MAX4239, a special "ultra-low offset/drift, low noise precision amplifier". Whew, what a mouthful!

As the name suggests, it's a pretty high spec device. The key figure in this application is the near-zero offset voltage. And not just "low offset" like many precision op-amps, this one has almost no practical offset voltage at all. 0.1uV typical, with a maximum figure of 2.5uV over the entire temperature range, if you want to know the actual numbers.


This class of op-amps are known as "auto-zero" (or "chopper") amplifiers.

Maxim are a bit hush-hush on the actual internal workings of their particular device, saying only "*These characteristics are achieved through a patented autozeroing technique that samples and cancels the input offset and noise of the amplifier. The pseudorandom clock frequency varies from 10kHz to 15kHz, reducing intermodulation distortion present in chopper-stabilized amplifiers.*"

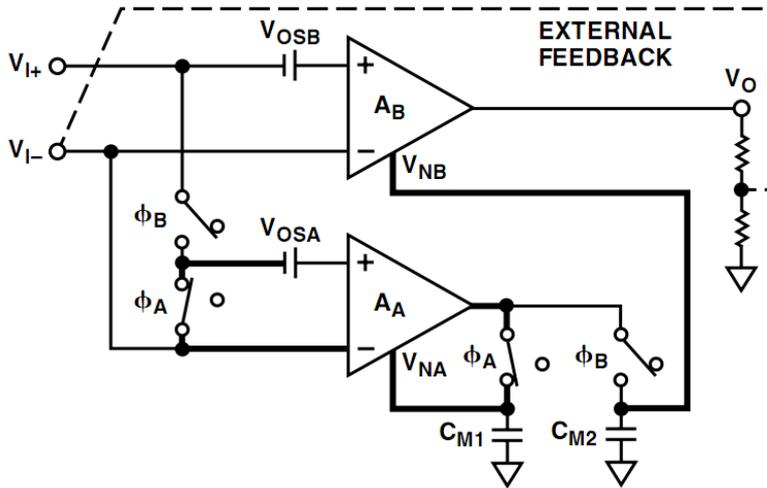But we can get a good idea of how a basic auto-zero amplifier works in the following diagram.



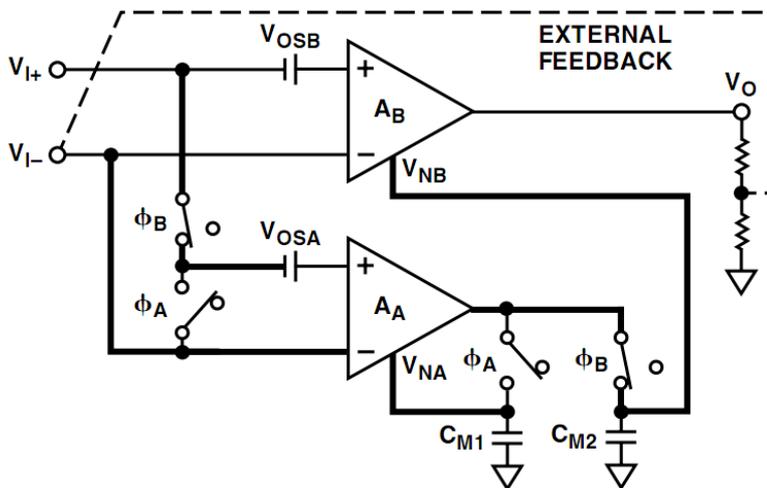a. Auto-Zero Phase A: null amplifier nulls its own offset.



b. Output Phase B: null amplifier nulls the main amplifier offset.

An auto-zero amplifier is basically the combination of a normal op-amp (A_B), with a “nulling” op-amp (A_A) that continually corrects for the DC offset voltage of the main amplifier.

So the device is driven by a clock (internal) that drives a two phase offset process.

In the first phase (figure a), the main amplifier (A_B) is offset with the voltage stored on capacitor C_{M2} . The nulling amplifier (A_A) measures its own offset voltage and stores it on capacitor C_{M1} .

In the second phase (figure b), the nulling amplifier (A_A) measures the input difference voltage on A_B and stores this value on capacitor C_{M2} , ready for the next cycle.

Using this process the offset voltage of the main amplifier is continually eliminated.

A side benefit of this is that it also eliminates typical op-amp $1/f$ noise, as the low frequency is treated as a slowly varying input offset voltage and hence gets cancelled out.

The pseudo-random clock used in the MAX4239 also helps to reduce the effects of intermodulation distortion as AC signals approach half the chopping frequency (10-15KHz).

This remarkable DC performance allows the μ Current to have insignificant output offset errors, and will display zero volts output for a zero current input.

It is also quite low power, around 600 μ A, thus allowing for battery operation from a small lithium battery. The supply voltage is specified down to 2.7V, making it ideal for operation from a single 3V lithium battery.

The MAX4239 also has a companion device, the MAX4238. The only difference is that the MAX4239 is a high bandwidth "decompensated" version of the MAX4238. The MAX4239 requires a minimum gain of 10 which we have in this circuit, so it's better to use the higher bandwidth device.

If you want to use the MAX4238 then that is possible without any circuit changes, only the bandwidth and other AC performance measurements will differ.

A fixed gain of 100 is defined by precision resistors R5, and R3+R11. These are 0.1% low ppm resistors that are accurate with negligible temperature drift.

R9 ensures output stability, as well as providing a useful jumper link for the single sided PCB layout. This value will be low enough to ensure error free operation with meters greater than around 100Kohm input impedance. If for some reason your meter is lower than this, than you'll have to lower the value of R9 appropriately.

Current Ranges

There are 3 current ranges that are defined by the shunt resistor on each range, and the gain of U1.

R2 (10K 0.1%) is the shunt resistor for the nA range and is permanently connected across the input terminals. It gives a burden voltage of 10 μ V/nA (1nA * 10K). The other shunt resistors R1 and R8 are disconnected in the nA range.

The purpose of having R2 permanently connected is to ensure that the input is not left open circuit.

R8 (10R 0.1%) is switched in parallel with R2 in the μ A range by SW1B which gives a burden voltage of 10 μ V/ μ A (1 μ A * 10R). R2 contributes a small error of less than 0.1% in this case.

R1 (10mR 0.5%) is switched in parallel with R2 in the mA range by SW1B which gives a (resistor) burden voltage of 10 μ V/mA (1mA * 10mR). Because R1 is such a low value, the solder joints and PCB tracks can contribute large errors, so a special purpose designed "shunt" resistor is used. This is a 4 terminal device that includes the 10mR resistor and two "sense" terminals connected directly across the resistor on the substrate. This eliminates any error caused by solder joint or PCB trace resistance.

However, the mA range is special because the shunt resistor is such a small value compared with the resistance of the range switch, that the switch will dominate the actual total burden voltage. The switch contact resistance is rated at 70 milliohms maximum, so the actual burden voltage on the mA range will vary from unit to unit, and will change with time, but can be taken as a nominal 70 μ V/mA.

The maximum current in the mA range is a nominal 300mA, as this is the contact rating of the switch. But in practice it can be higher than this.

You will notice that the virtual ground is connected to the sense side of R1, this means that the sense voltage for R2 and R8 also flow through this terminal, but the sense current in these cases is negligible so it has no effect.

SW1A selects which shunt resistor gets fed through to the amplifier.

Power Supply

Any current adapter must be able to handle both positive and negative inputs, and thus a dual polarity power supply is required. In a battery powered device, this can be achieved in one of three ways.

The first is by using two or more series batteries providing a middle "0V" tap. This is very convenient, but takes more space, there are more batteries to replace, and you can get uneven drain from the batteries thus making true low battery detection more difficult.

The second is by using a single battery supply and generating a negative supply using say a switched capacitor inverter. This is convenient for low current applications, but it generates noise and requires filtering. Also, using a 3V lithium battery means a total power supply voltage from 5.4V to over 6V. But our MAX4239 can only handle a maximum 5.5V supply voltage, so extra diodes would be required.

The third method involves a "virtual ground" split supply circuit, and this is what is used in the μ Current. The circuit comprises U2, R6, and R7. R6 and R7 split the battery supply in half, and U2 buffers this to provide a low impedance output.

U2 is an LMV321, a general purpose low power low voltage op-amp, essentially a low voltage version of the venerable LM351. Power consumption is a measly 130uA, with R6 and R7 taking another 13.5uA or so.


R10 is used to ensure output stability.

The output from R10 is now the "virtual ground" reference for the rest of the circuit. Thus ensuring U1 has a +/-1.5V supply from the battery, and the input current shunt resistors can now sense current in either direction.

Low Battery Detection

To ensure that what you read on your multimeter is accurate, it is important to know if the battery voltage is low and thus possibly affecting the measurement.

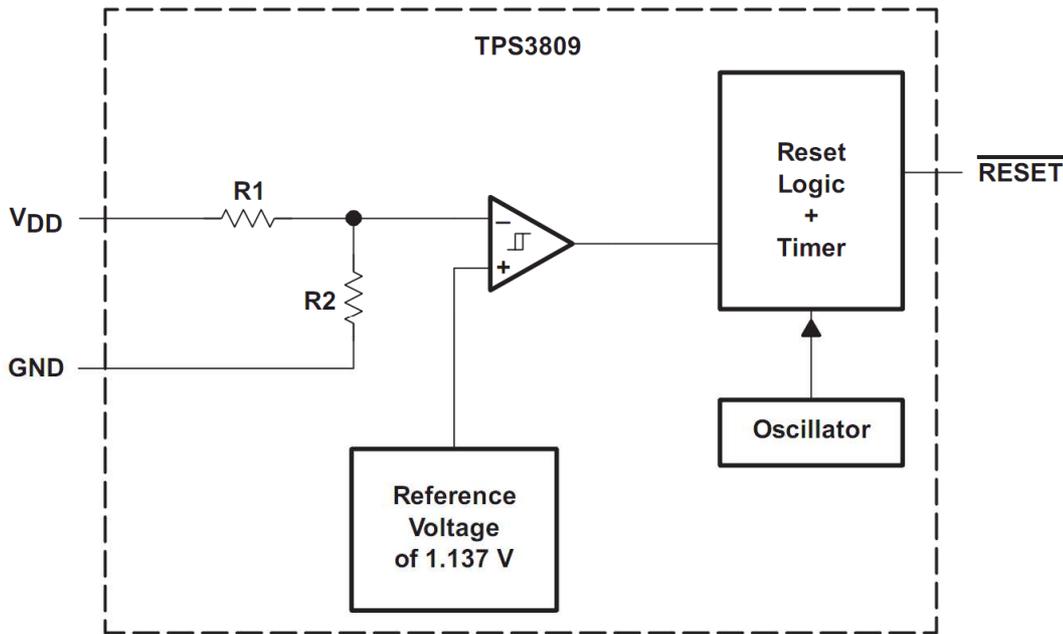U3 does this job very neatly and accurately in a single chip. It is a Texas Instruments TPS3809L30 "Supply Voltage Supervisor"




You can see how it works in the accompanying functional diagram. There is a precision resistor divider, voltage reference, and an output circuit with timer.

If the input voltage on the VDD pin drops below 2.64V then the RESET output will go LOW.

In our application, /RESET will be HIGH and thus the BATT LED will be ON if the battery voltage is above 2.64V. Conveniently, this is about the “dead” point for a 3V coin cell lithium battery which spend most of their operational life around 2.7 to 3.0V.

● Discharge Characteristics

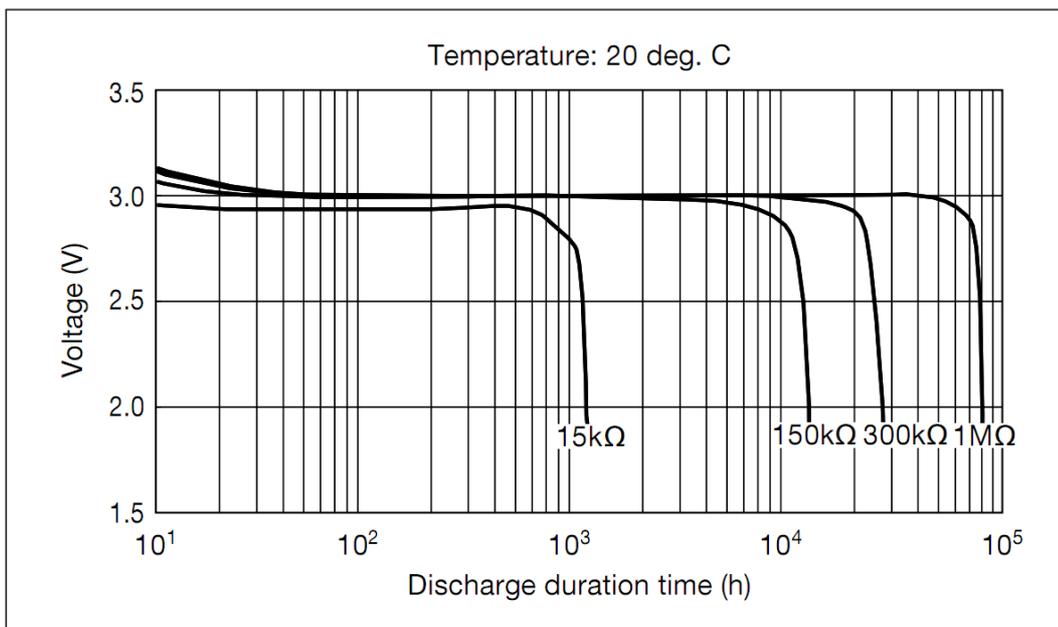

Making use of the same DP3T switch used for the current range selection we are able to get a very handy “battery check” mode between the ON and OFF modes that switches in U3 to light the LED.

You can keep using the μ Current in this mode with the LED ON if desired, it simply uses more battery power.

The in-built timer will take about 0.2 of a second to light the LED, so it's possible to move the power switch through the BATT CHECK mode and not have the LED light if you are quick enough.

Output Voltage Range

The MAX4239 is a rail-to-rail output device, so is capable of fairly close to the supply rails on the output. Given that the power supply will be at least $\pm 1.35V$ for a working battery, that allows for an output voltage that approaches this figure within a few millivolts.

Normally though the μ Current will be used with your multimeters mV range which will be typically up to a maximum of 999.99mV for a 10000 count meter. So there is some head-room left if you want to push it higher for any reason.

Output Units

The output units are scaled by the shunt resistors and gain of U1 to be precisely 1mV per range unit. So the output will be 1mV per mA, 1mV per μA , or 1mV per nA.

This makes it easy and logical to directly read on your multimeters mV range. So if you read 100mV on your meter, that equates to 100mA, 100 μA , or 100nA depending upon the range you have selected.

AC Performance

The AC performance is shown in the accompanying screen shots as measured with an Audio Precision analyser with a 1V output level on the μA range. There is little performance difference between the ranges.

The nominal bandwidth is 2KHz, as the THD starts to increase exponentially after this. This figure is quite sufficient as most meters have a 1KHz response on AC current ranges.

Overloads

Fuses have been omitted from the design to ensure as low a total burden voltage as possible. Therefore you must be careful to ensure that the input is not connected directly across a supply voltage capable of providing a current that exceeds the selected range. Failure to take care here can result in a blown shunt resistor.

Connectors

The connectors are standard 4mm banana plugs, with standard 19mm spacing. This allows the use of various types of adapters if required. The screw terminal type connectors are used for the current input, which is convenient for connecting to existing wiring without test leads. The top screw part can be completely removed to enable some short "shrouded" banana plug test leads to fit.

Construction

Apart from the connectors and switches the entire design uses surface mount components. This was done in order to give a professional look, and reduce cost and size by using a standard UB5 Jiffy box.

The PCB is used as a replacement for the jiffy box front panel and this provides a very elegant and durable appearance.

The PCB used in the prototype is a double sided board mainly for the purpose of improving the red solder mask finish. The shield plane on the top layer is connected to VGND.

All components are relatively large 0805, SO and SOT packages so soldering is pretty easy using a basic iron. See the March 2008 issue of Silicon Chip for an article on how to solder surface mount components if you are new to this.

There are a few things that make SMD hand soldering much easier. A small chisel point tip (not conical), fine multi-core solder (0.56mm or better), and a pair of fine pointed tweezers. If you have these things then hand soldering is a cinch.

Start with the three IC packages, making sure of correct polarity on U1. Follow with the passive resistors and capacitors, taking extra care with the precision resistors not to damage them with excess heat.

Applying a small amount of solder to one pad first makes it easy to “reflow” the component into place while you solder the other end.



Next solder on the LED. This is a special “bottom emitter” LED which is effectively soldered in upside down, with the light coming through a cutout in the board. Be sure to match the polarity to the silkscreen.

Next solder the battery holder into place ensuring the correct polarity. Apply the iron and then solder to the top side of the flat pin instead of the pad for this part. The solder should then reflow easily to the pad underneath.

Turn the board over and install the two slide switches ensuring correct orientation. If you have the vertical switches then the side with the metal indent should face to the outside edge of the board. Side mount switches should have the switch lever towards the middle of the board. Ensure the switches are flush with the board and aligned straight. Tack one pin down first to check before soldering the rest.

Finally the banana connectors. Unscrew them completely first, removing all nuts, washers and solder tags. Install them on the top side with just the plastic spacers touching the top side of the PCB. Next put the solder tag on the bottom side and solder it *only* to the smaller adjacent solder pad. Then place the washer and screws on top and tighten. Feel free to add a thread-locker and/or glue if desired.

μ Current - Rev 2
(c)2009 David L. Jones

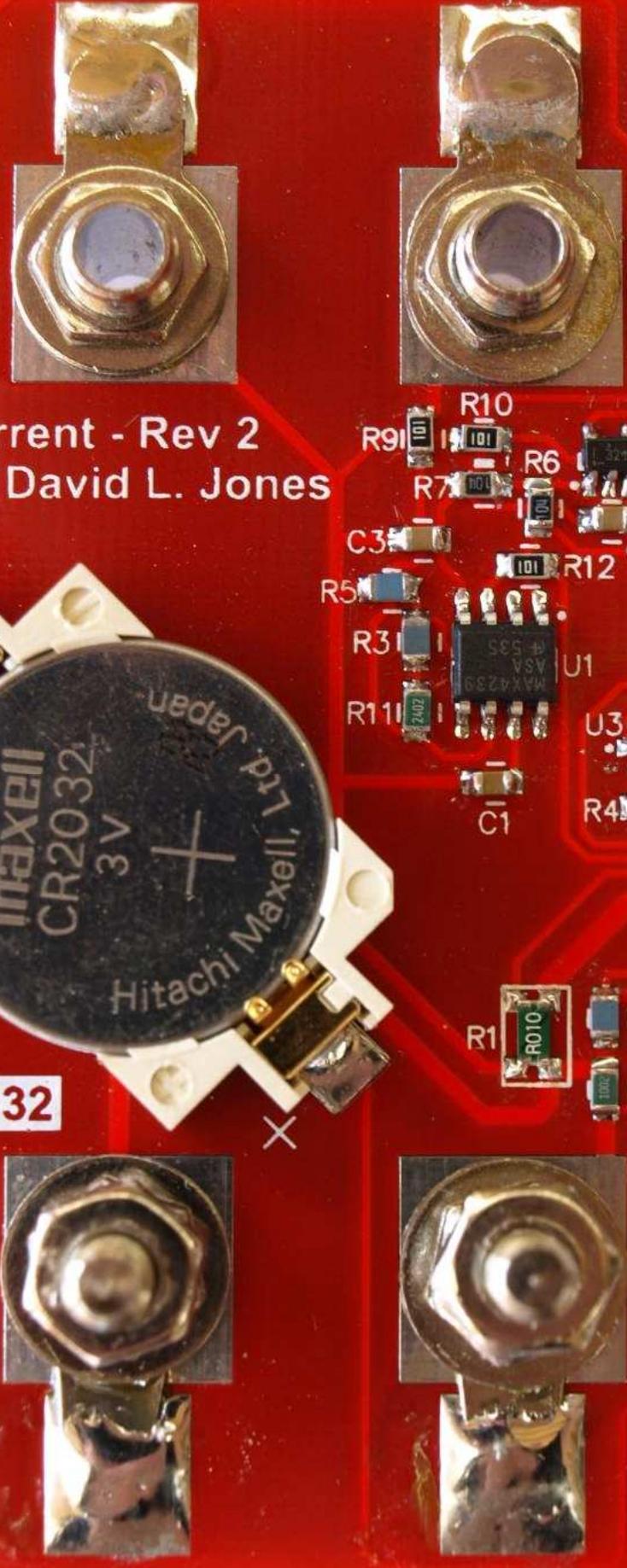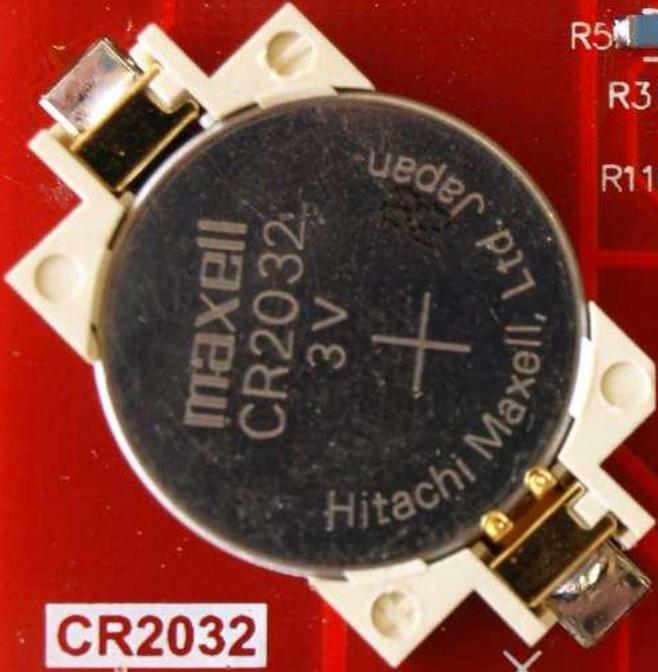

Testing

Testing is fairly straightforward. You will need a power supply and some suitable resistors (or decade resistance box), and your multimeter.

Insert the battery and switch to BATT CHECK mode. The LED should light within 0.2 seconds. Switch to ON mode and the LED should turn off.

Measure the DC voltage from the negative output connector (VGND) to one then the other side of the battery in order to check the split supply system. You should get approximately +/-1.5V and both values should match closely.

Connect the Voltage Output terminal to your multimeter set to the mV DC range. With nothing connected you should measure zero on all three current ranges.

Select a resistor suitable for each range to give you a decent current level around say half of your meters full scale. E.g. for a 5V supply, use a 47R 1W (106mA), 47K (106 μ A), and five 10M resistor in series (100nA).

Connect your test resistor in series with your supply and the Current Input terminals. Ensure that you have the correct range selected before switching on your supply voltage, you don't want to blow any shunt resistors!

Your meter should read approximately 106mV (mA), 106mV (μ A), and 100mV (nA) for the values mentioned. You can double check your values by measuring the actual resistor values and supply voltage and calculating the current if desired.

If these currents match then your μ Current is ready for operation, as the "calibration" is inherent within the precision 0.1% components used.

The output value should not differ between BATT CHECK and ON modes.

It might be handy to check the battery current also. It should be around 0.7mA with the LED off, and around 3mA with the LED ON.

Don't forget to switch OFF when you are finished measuring.

The last step is simply screwing the PCB onto the box. With typical infrequent use the battery should last many years.

That's all there is to it, you now have a precision current measurement tool ready for those more demanding modern applications.

I hope this article has got you thinking about the impact burden voltage can potentially have on your current measurements.

Blank PCB's, kits, and fully built units are available from the authors web site.




*Using the μ Current to measure current drain of the author's μ Watch.
(Guess where the name came from?...)*

Specifications


- 3 Current ranges:
 - +/- 0-300mA (70 μ V / mA burden voltage typical)
 - +/- 0-1000 μ A (10 μ V / μ A burden voltage)
 - +/- 0-1000nA (10 μ V / nA burden voltage)
- Output Voltage Units:
 - 1mV/mA
 - 1mV/ μ A
 - 1mV/nA
- Resolution (nA range): 100pA (3.5digit meter), 10pA (4.5 digit meter)
- Accuracy (typical): <0.2% on μ A and nA ranges, <0.5% on mA range.
- Output Offset Voltage: Negligible on 4.5 digit meter
- Bandwidth: 2KHz nominal (+/-0.1dB)
- Temperature Drift: Insignificant over normal ambient range
- Noise: < -90dBV
- THD: < -60dB
- Battery: CR2032 Lithium coin cell
- Battery Life: >200 hours (LED OFF), >50 hours (LED ON)
- Connection: 4mm banana, screw terminal inputs, standard 19mm spacing

Parts List


100R 1% 0805	3
100K 1% 0805	2
470R 1% 0805	1
LVK12R010DER 10mOhm 0.5% 1206 Current Sense	1
1K 0.1% 0805	1
75K 0.1% 0805	1
24K 0.1% 0805	1
10K 0.1% 0805	1
10R 0.1% 0805	1
100nF 0805 Capacitor	3
C&K JS203011AQN DP3T Slide Switch PCB R/A	2
CR2032 Lithium Battery	1
1060TR CR2032 SMD Battery Holder	1
LTST-C230GKT 1206 Reverse Green LED	1
MAX4239ASA+ SO8 Opamp	1
LMV321AS5X SOT23-5 Opamp	1
TPS3809L30DBVR SOT23 Voltage Monitor	1
4mm Black Banana Jack	1
4mm Red Banana Jack	1
4mm Black Binding Post	2
4mm Red Binding Post	2
UB5 Jiffy Box Black	1

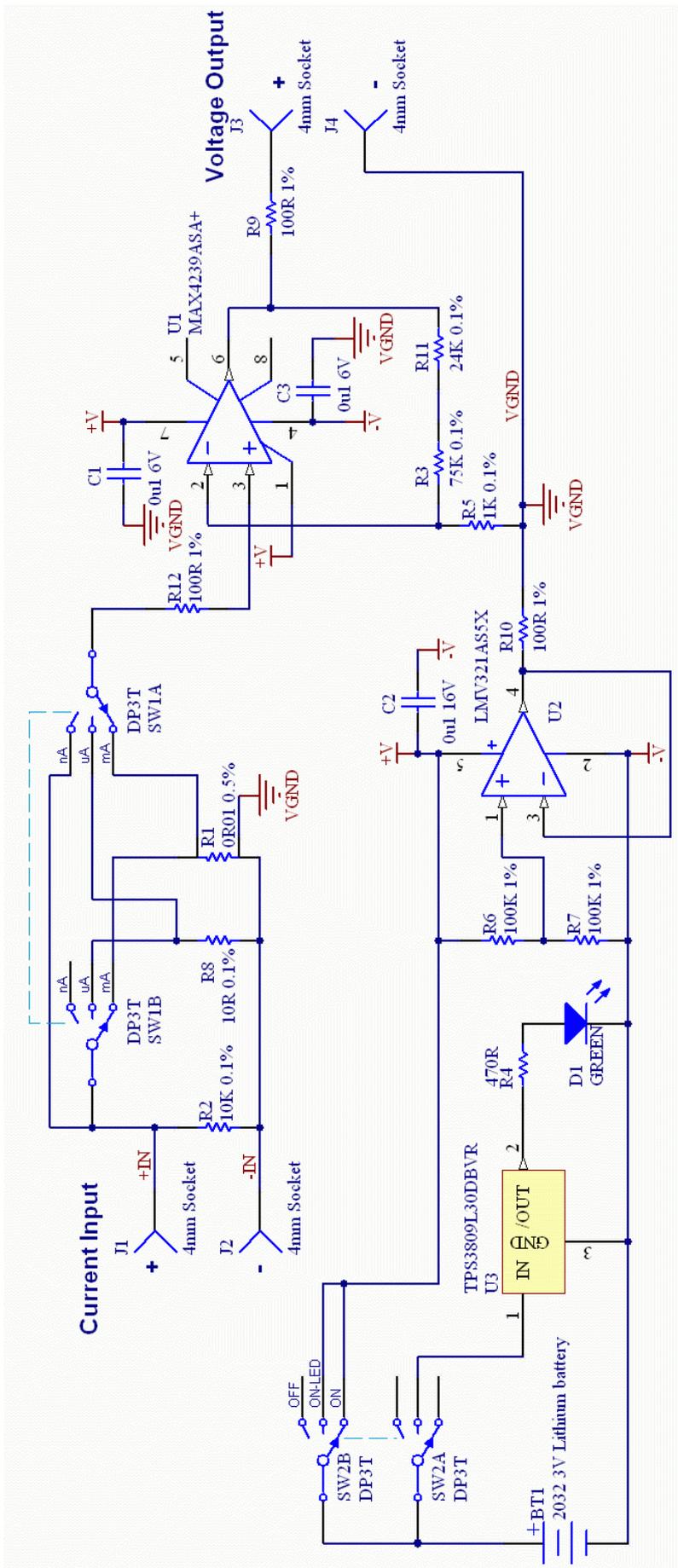


Complete Schematic Diagram

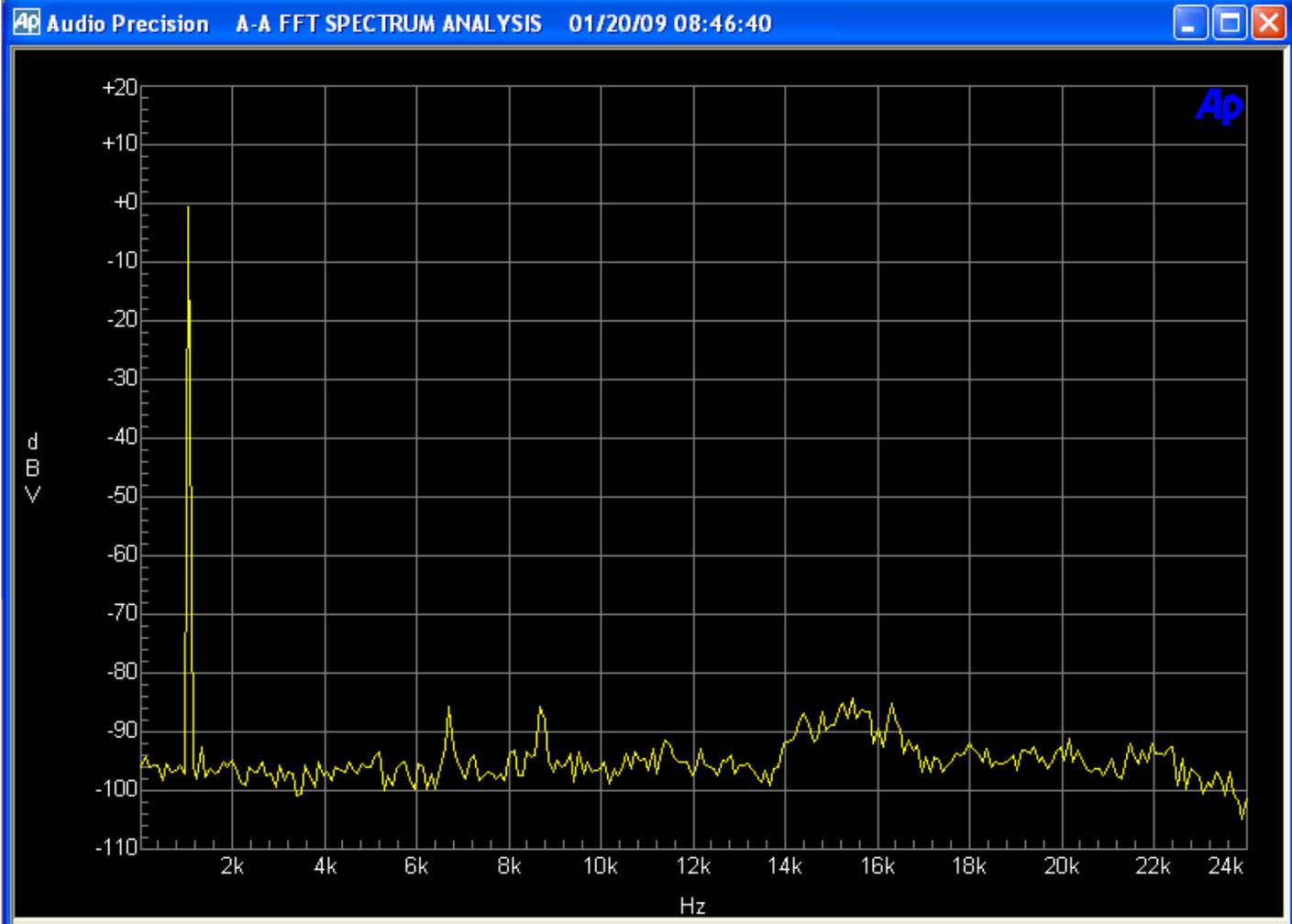

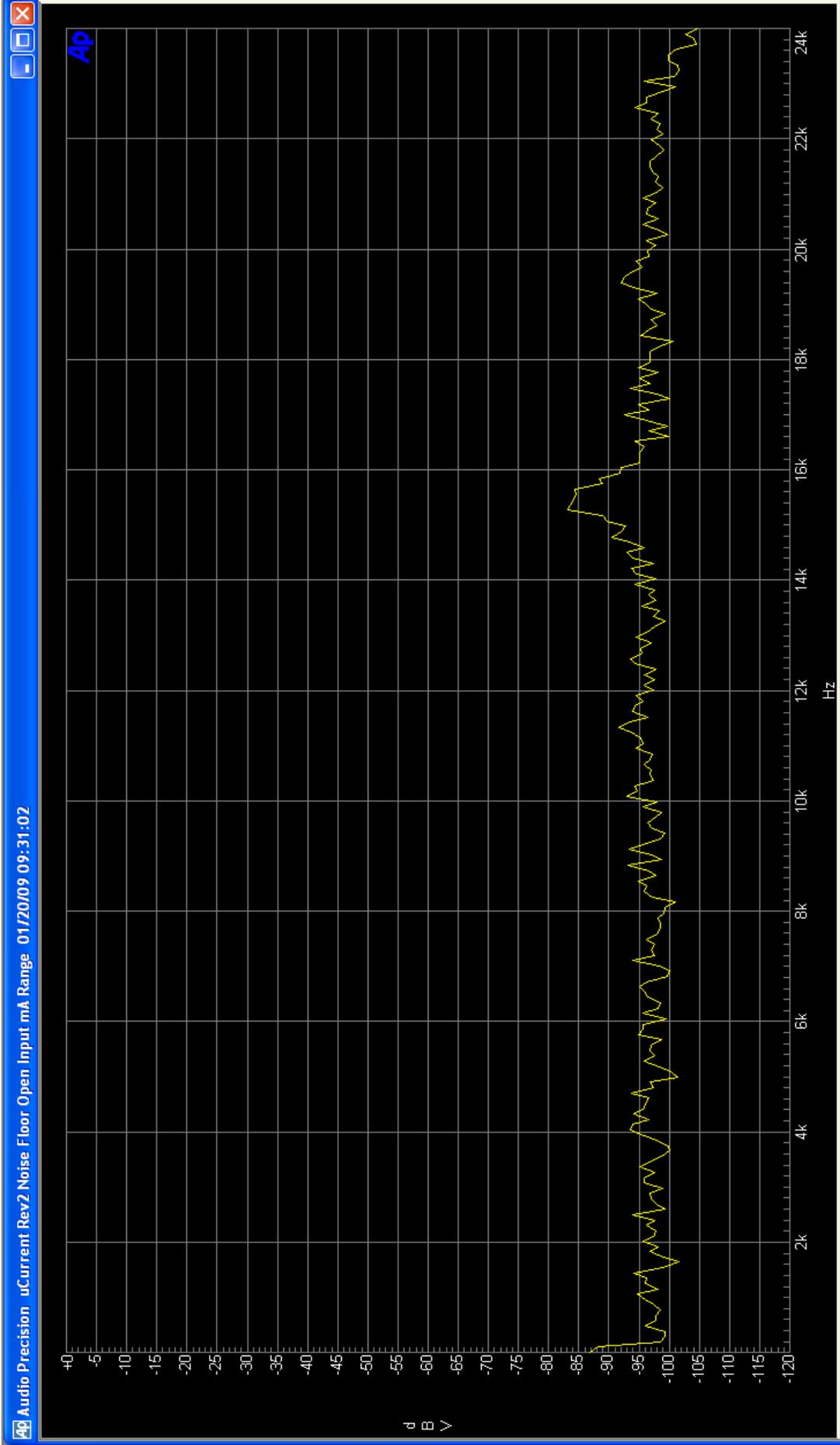FFT Spectrum with a 1kHz signal on the uA range.



Noise Floor mA range

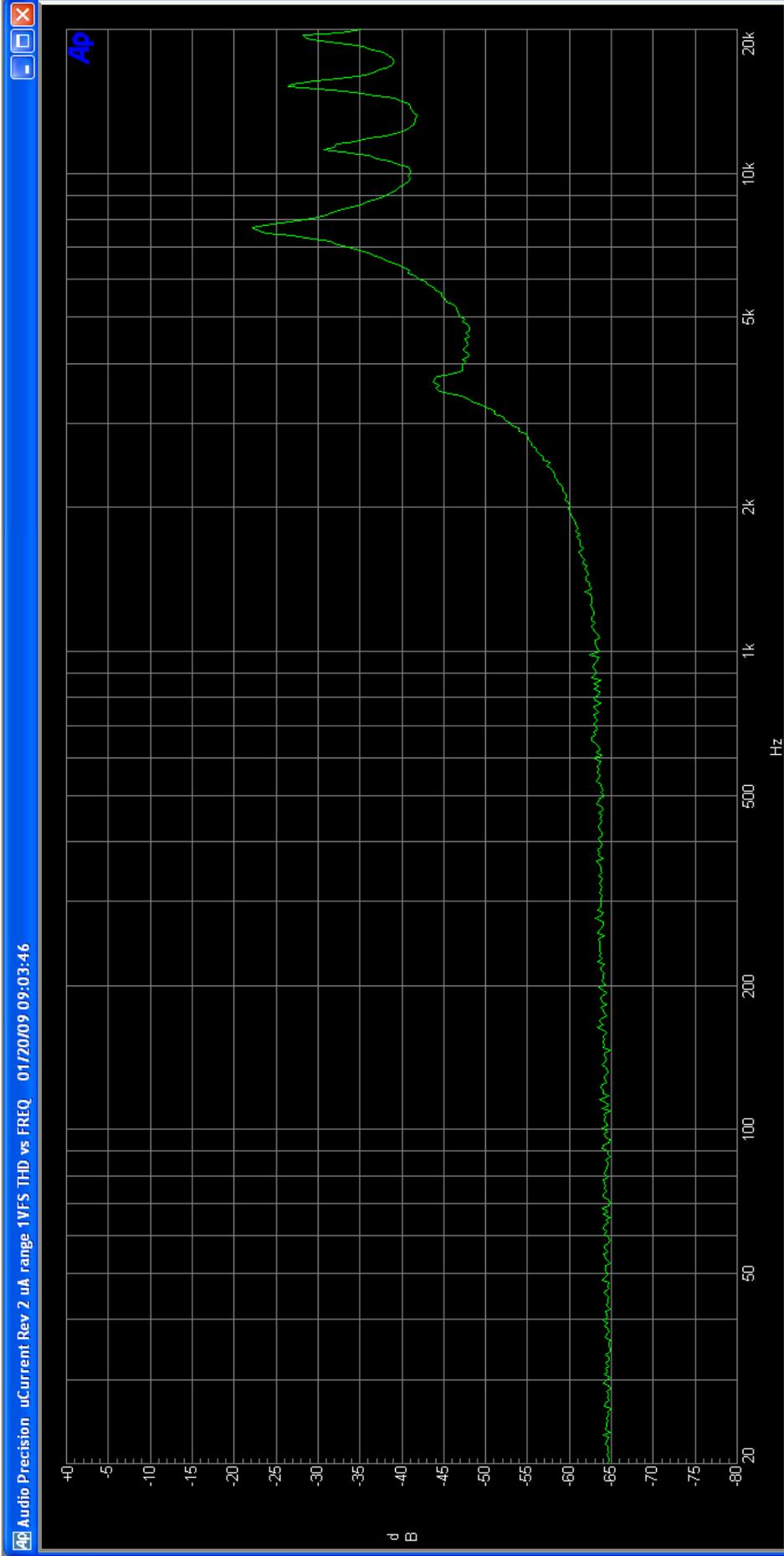

THD vs Freq on the uA range