



Drawing from Multisim so some stuff
have wrong names.

I do not know value of bipolar caps
So values just guess work

C16, C11, C9

D6 I guess that is 1N4148

D11 is M7 (1N4007?)

Q3 is 2SB647

DB1 is KBP307

PS: It does not work correctly in multisim,
so I hope I did not make any mistakes.