

AN11566

Driving an LED backlight, a buzzer, implementing a charge pump and a low-power system by the PCF8551 and PCF8553

Rev. 1 — 27 June 2014

Application note

Document information

Info	Content
Keywords	PCF8551, PCF8553, buzzer, charge pump, power-on reset, driving LED backlight
Abstract	The PCF8551 and PCF8553 devices are capable of driving a backlight LED and/or an electroacoustic converter like a buzzer or speaker circuit. Additionally a simple charge pump for low supply voltage operation is sketched out. The application note lists some variants of implementing these features.



Revision history

Rev	Date	Description
v1	20140627	initial version

Contact information

For more information, please visit: <http://www.nxp.com>


For sales office addresses, please send an email to: salesaddresses@nxp.com

1. Introduction


The PCF8551 and PCF8553 devices are capable of driving a backlight LED (see [Section 3](#)) and/or an electroacoustic converter like a buzzer or speaker circuit as described in [Section 2](#). The application note lists some variants of implementing these features. Additionally a simple charge pump for low supply voltage operation is sketched out in [Section 4](#). A hint on a reset circuitry is provided in [Section 5](#).

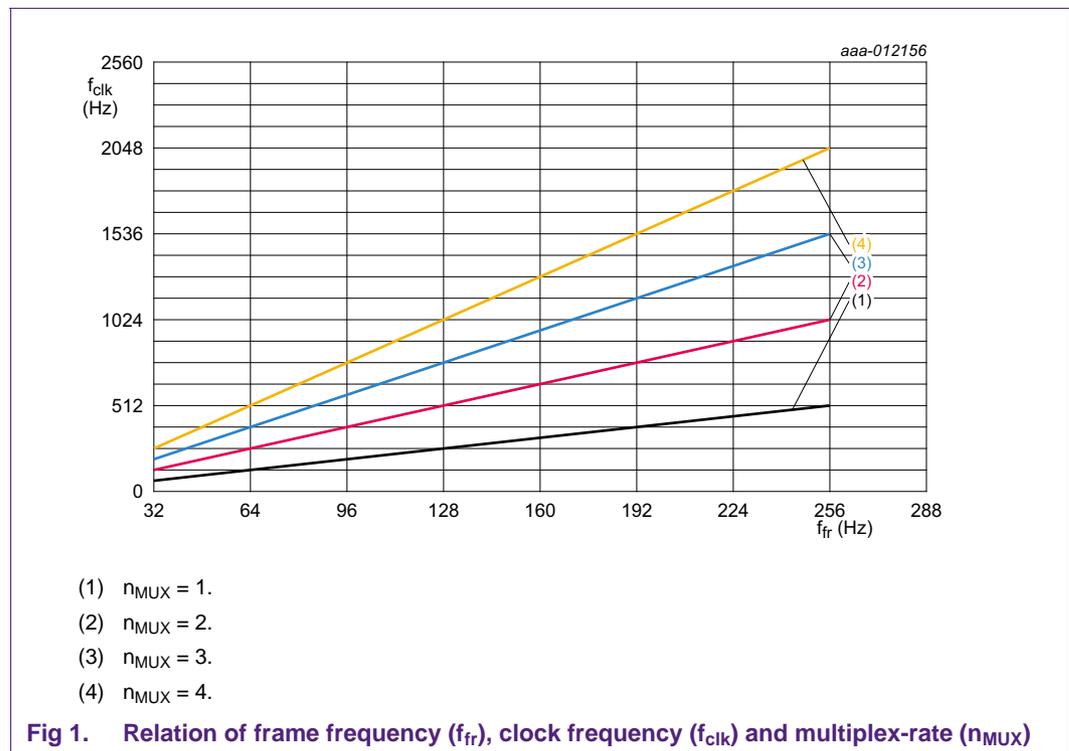2. Buzzer

The internally generated clock signal can be fed to pin CLK, which is then used as a digital output driver. As the clock frequencies are all within the audible range of 64 Hz to 2048 Hz and the output driver is able to deliver a reasonable amount of power, the clock signal can be directly fed to an electroacoustic transducer. Attenuation of the signal, if necessary, is easily achieved by adding a series resistor or capacitor. Output frequencies are controlled according to the combination of frame frequency and multiplex rate as shown in [Figure 1](#). They are not independent of the requirements posed by the display, which should be given preference. For details, see the individual data sheets of PCF8551 and PCF8553 respectively.



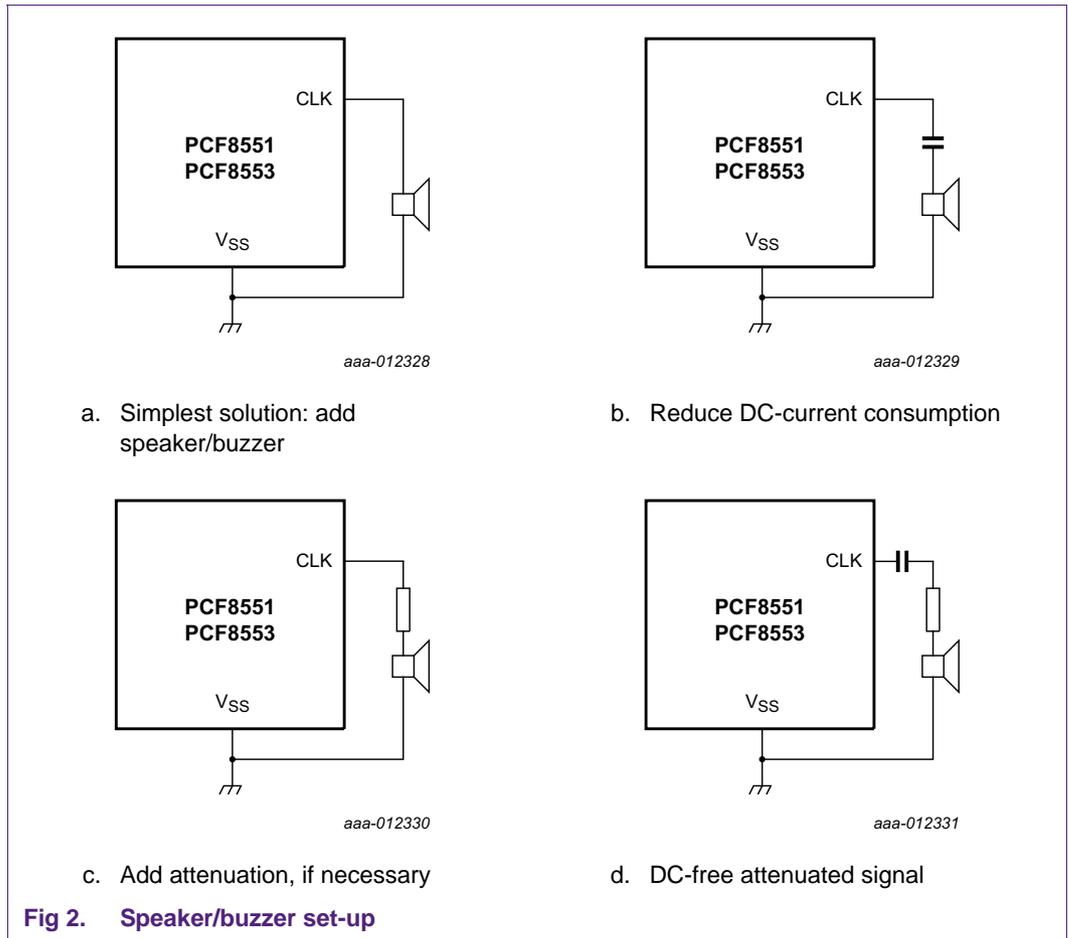The clock frequency is set by writing to registers 01h and 02h. To feed the clock-frequency to the output, the COE bit must be set to logic 1.



Experiments with an 8 Ω speaker showed reasonable performance. It is also possible to drive a capacitive buzzer.

3. Backlight control

3.1 Basic solution

Figure 3 shows a simple backlight control limited to only turning the light on or off. The CLK output is able to drive one white LED without issues.

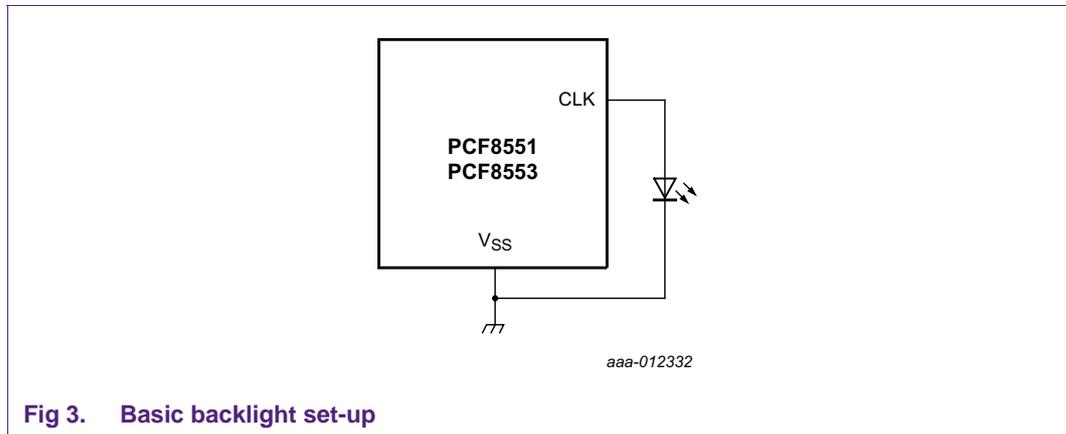


Fig 3. Basic backlight set-up

3.2 Solution with brightness control

In Figure 4 an N-channel MOS transistor T1 is used to drive a white LED. Its gate is controlled by a segment output to adjust brightness. Figure 9 shows the associated waveforms for SEGn.

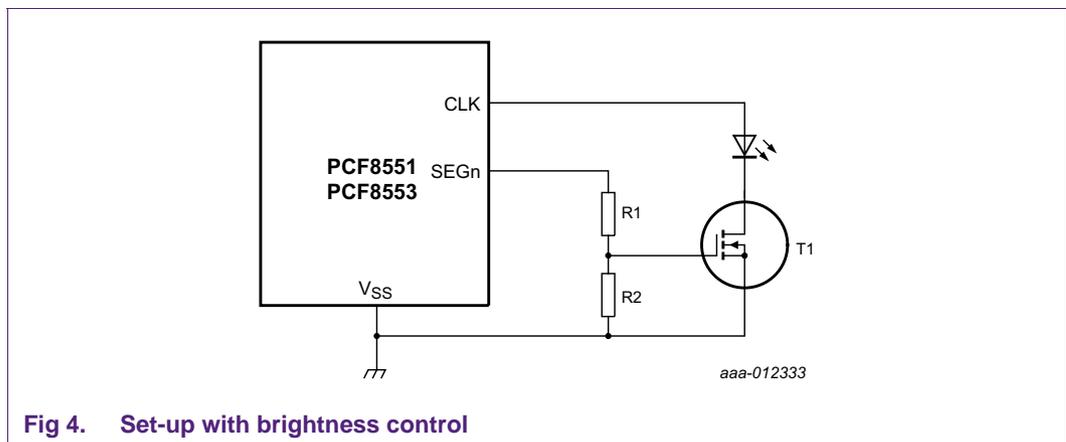


Fig 4. Set-up with brightness control

In this example, the backlight is turned on by enabling the CLK output. By adapting the switching level V_{SW} to the threshold V_{th} of T1, appropriate brightness control can be achieved. Resistor values must be in the several $M\Omega$ ranges to limit current loading. V_{OD} is the overdrive voltage at the gate for the transistor to deliver the appropriate amount of drain current.

$$V_{SW} = \frac{R1 + R2}{R2} \times (V_{th} + V_{OD}) \tag{1}$$

In the example of [Section 3.4](#) a multiplexing of 1:4 is used with the switching level V_{SW} placed close to V_{LCD} . If more than one LED is supposed to be driven, they must be connected to V_{LCD} . T1 must be able to cope with the associated load current.

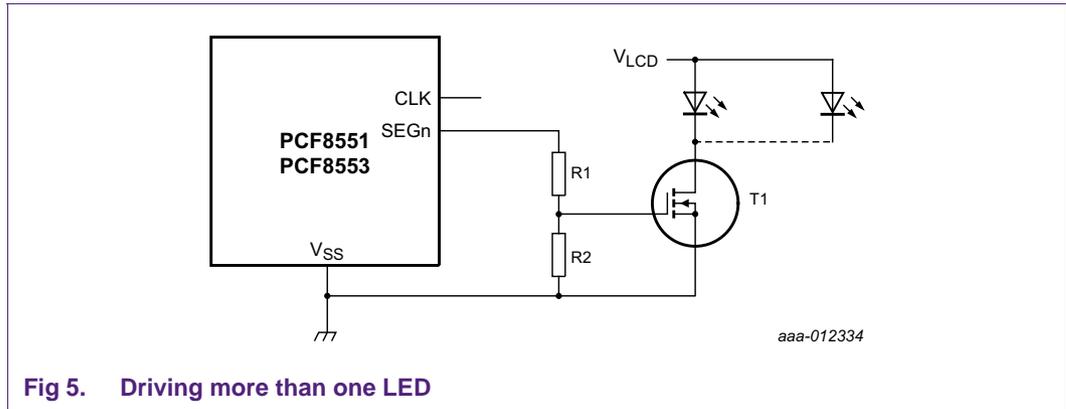


Fig 5. Driving more than one LED

Potentially a temperature compensation needs to be implemented, because V_{th} decreases with temperature, a fact, which might be canceled by adding a diode within the voltage divider. On the other hand, the current drive capability of T1 decreases with temperature. The voltage divider must be adapted appropriately.

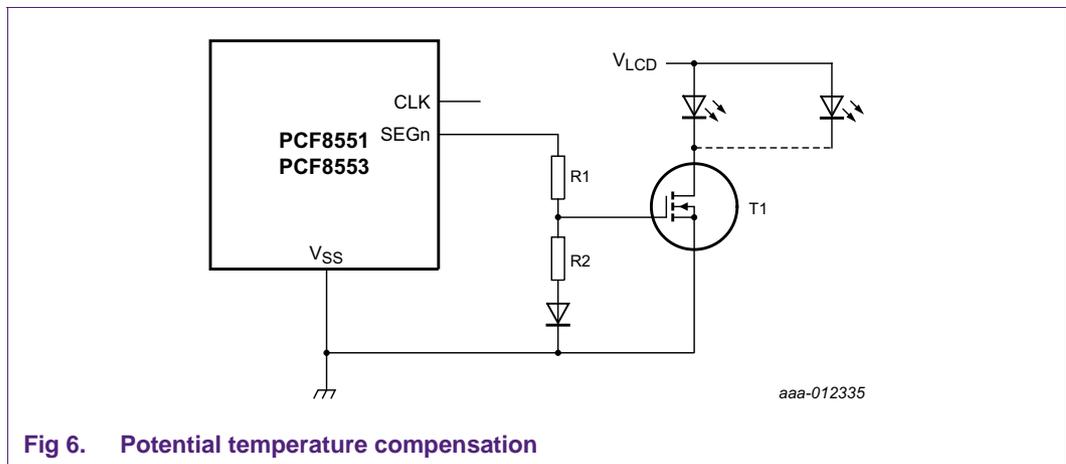


Fig 6. Potential temperature compensation

3.3 Multi-color with brightness control

For backlights, providing individual control of separate LEDs for red, green, and blue, the amount of individual color can be controlled by separate segment outputs, in case they are not required for the normal display function.

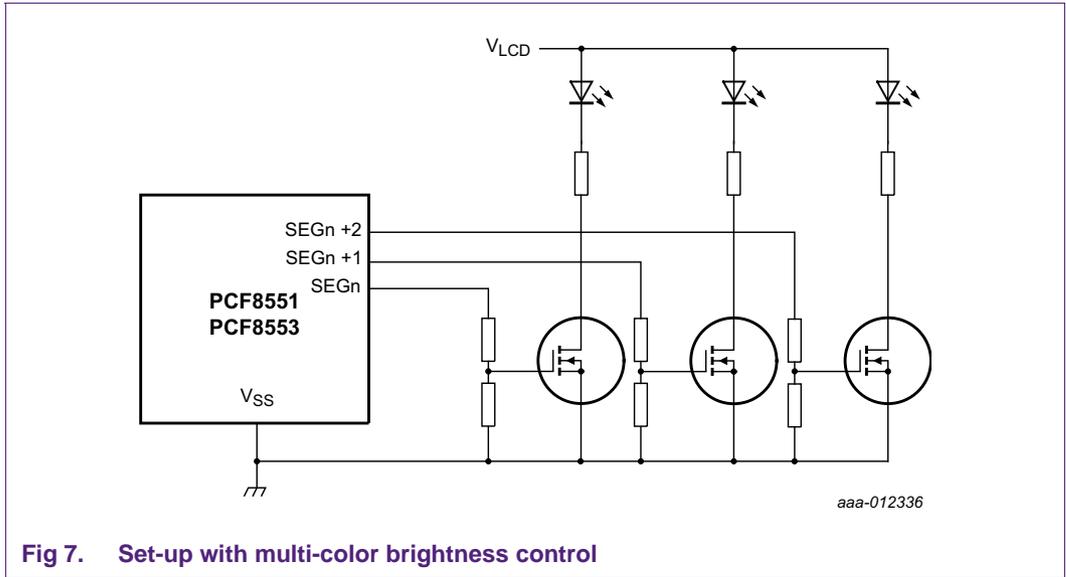


Fig 7. Set-up with multi-color brightness control

3.4 Case of application

In a case of application, it was possible to drive a DE LP-301-RGB backlight by DISPLAY Elektronik GmbH. This comprises of 3 LEDs, a red, a green, and a blue one, which combined, result in white backlight, but they can also be driven individually to change colors.

3.4.1 Schematic and elements

A BS170 N-channel MOSFET was used to drive the backlight. The gate was controlled by segment 0, which was also fed to the display for verification. In practice, an unused segment should be used for this purpose. V_{LCD} was set to 5 V to match the display as well as the backlight requirements. Due to its lower threshold voltage, the red LED needs a series resistor to match the brightness levels and adjust color temperature.



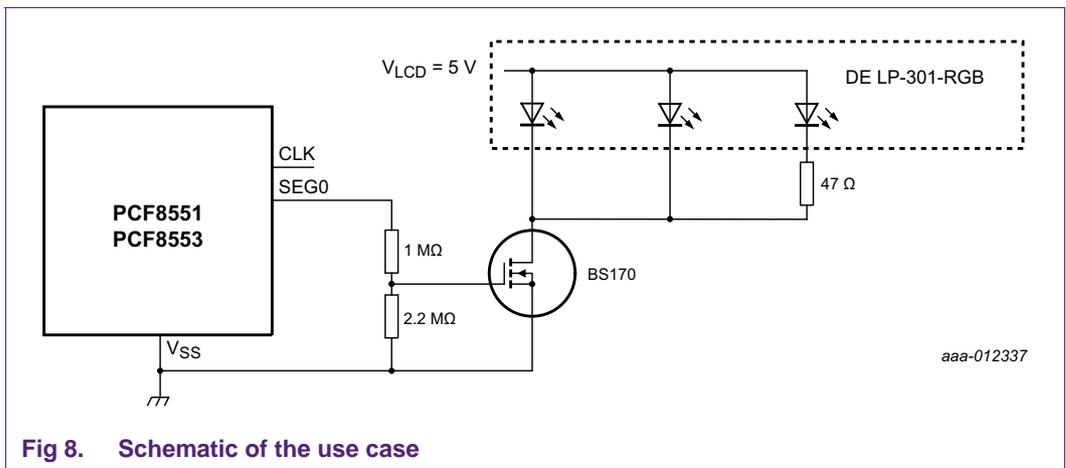


Fig 8. Schematic of the use case


The threshold voltages for green and blue are specified to be 3.1 V, while it is 1.9 V for the red light. Typical current consumptions are 15 mA, 15 mA, and 10 mA respectively; so a total amount of 40 mA must be provided. Due to the duty cycle of the segment signal, this requires a peak current of ~80 mA for the BS170.

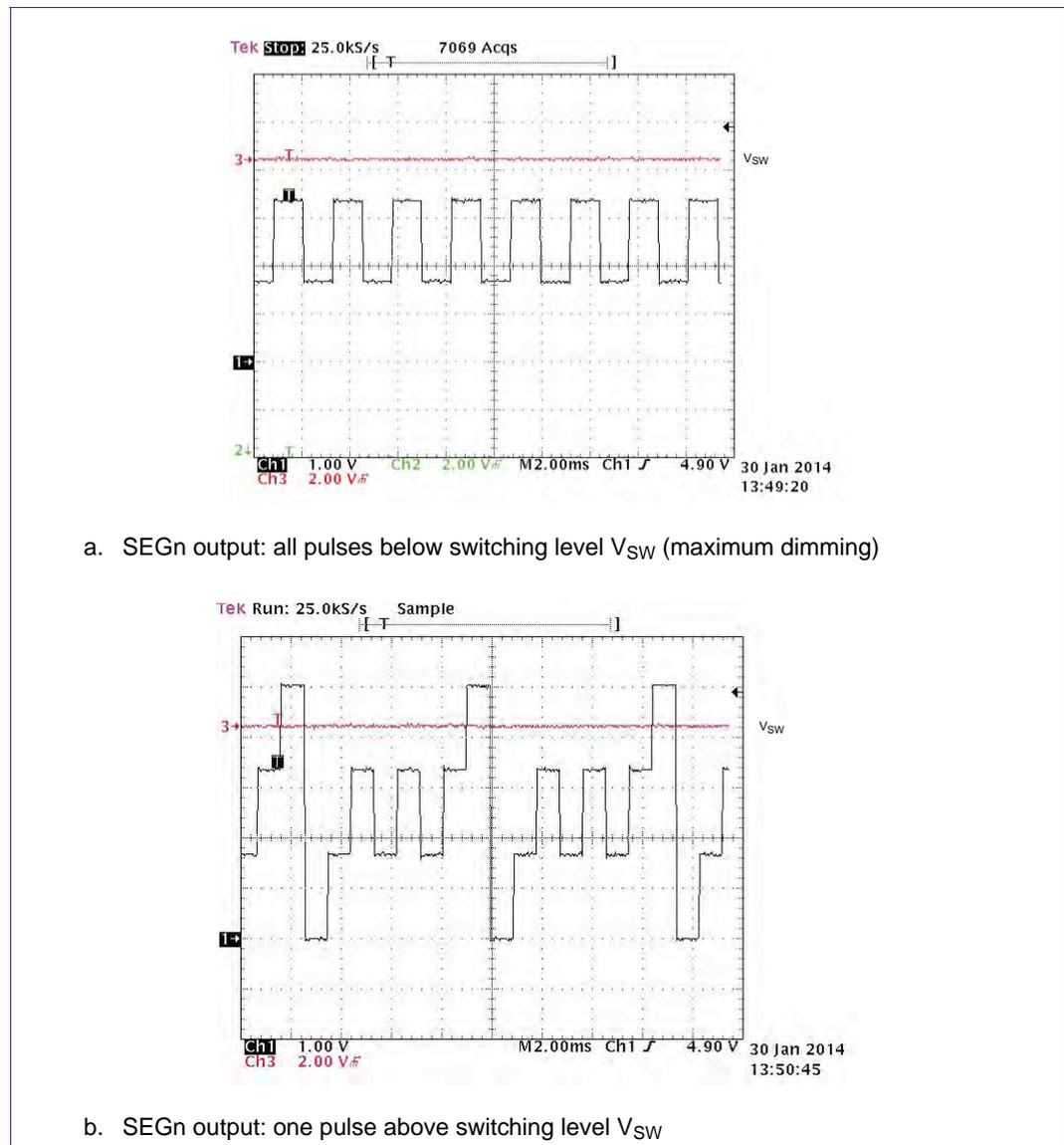[Figure 9](#) depicts the waveforms at the segment output, while [Figure 10](#) shows the performance when running through the individual brightness control steps.




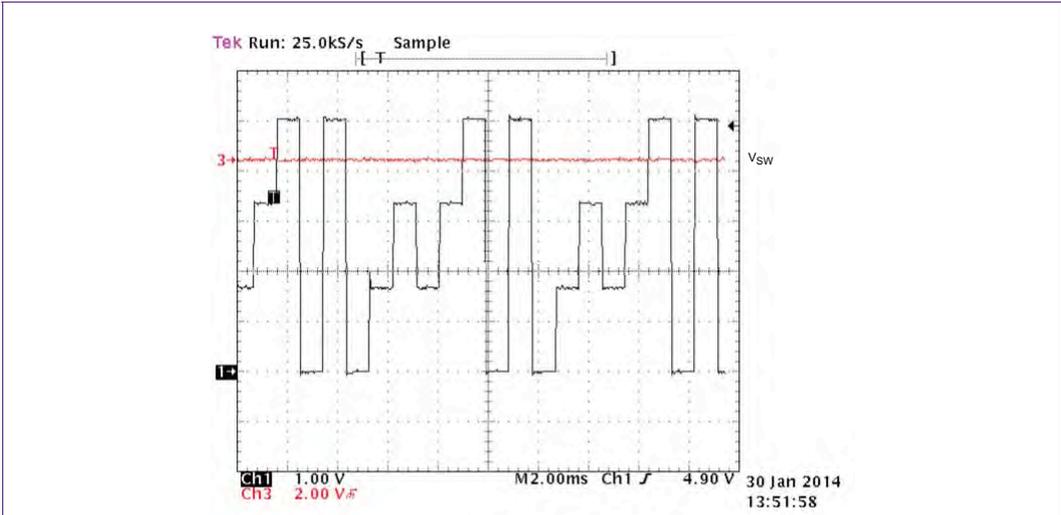


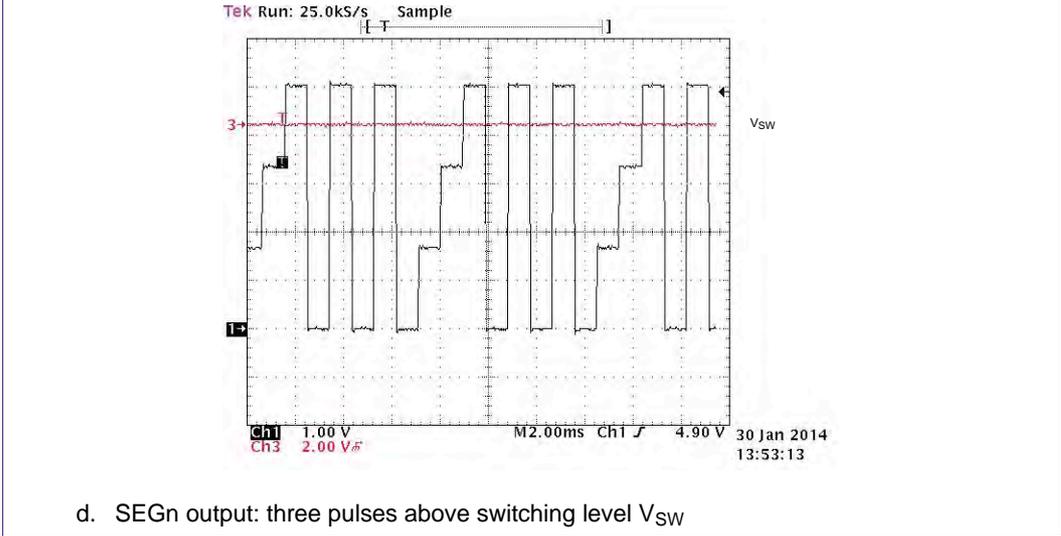c. SEGN output: two pulses above switching level V_{sw}



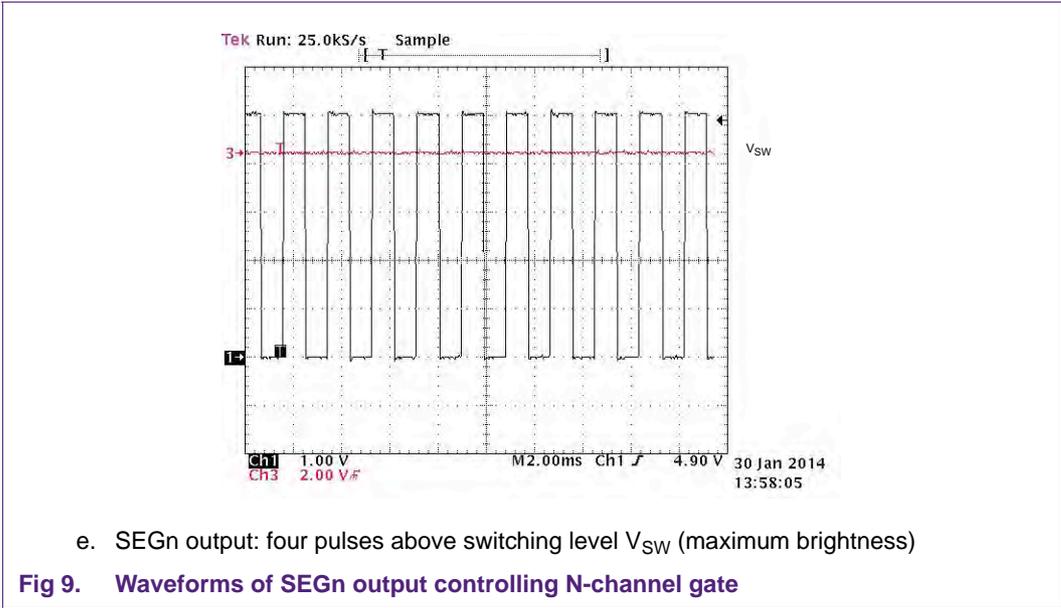
d. SEGN output: three pulses above switching level V_{sw}



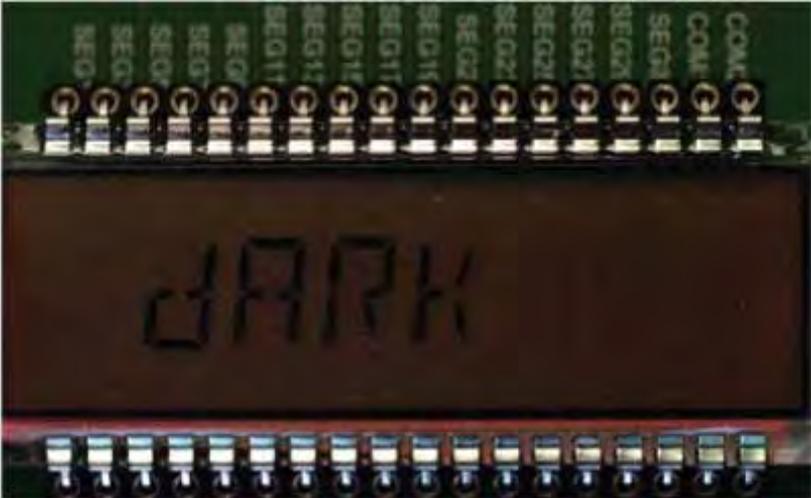

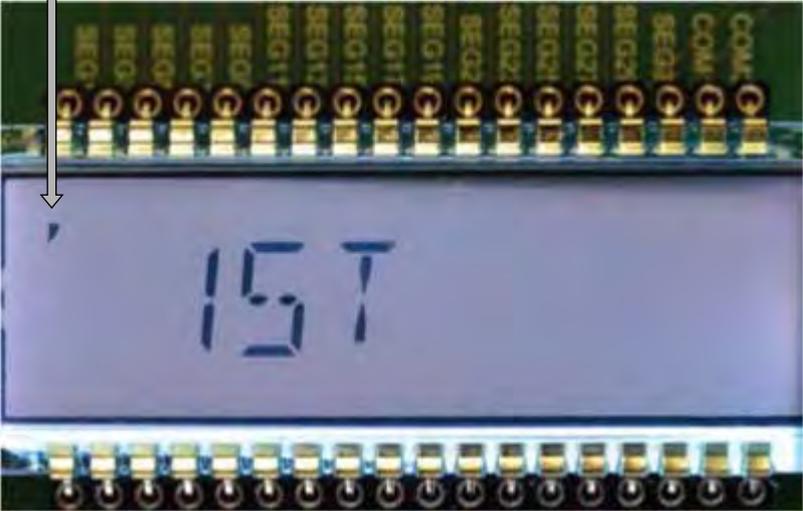
a. Maximum dimming

Brightness control by SEG0.
This should be done by an
unused segment in practice




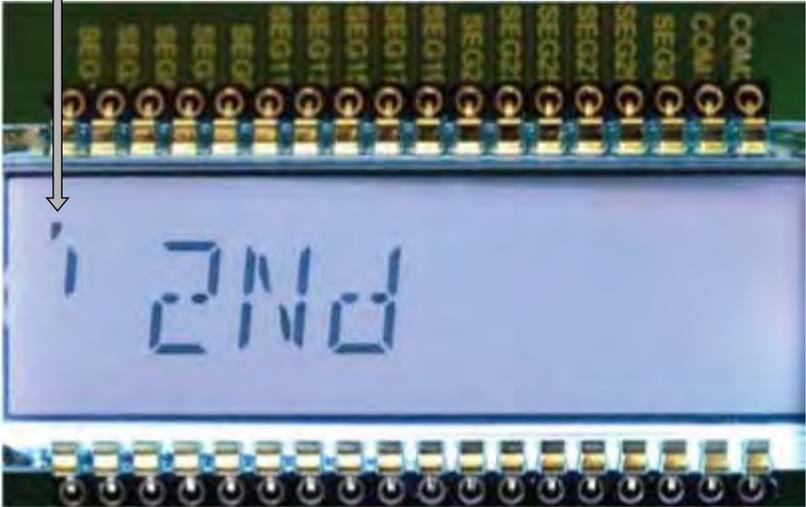b. First step of brightness control


Brightness control by SEG0.
This should be done by an
unused segment in practice



c. Second step of brightness control

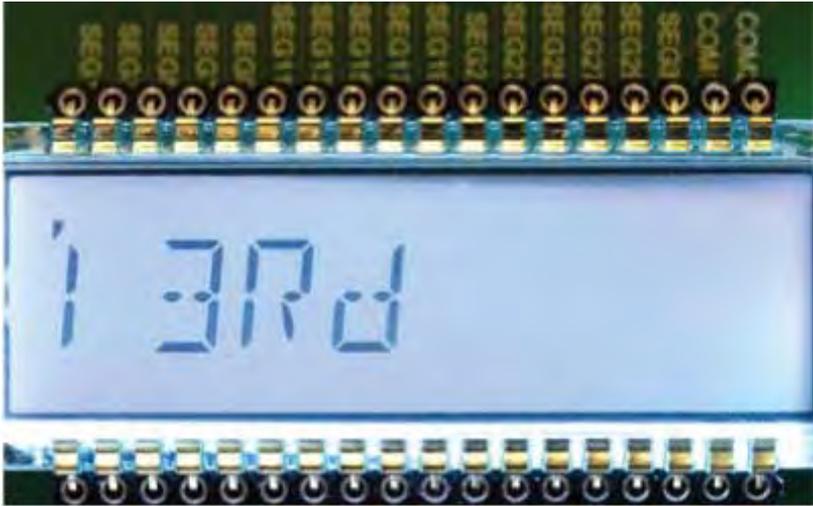

d. Third step of brightness control

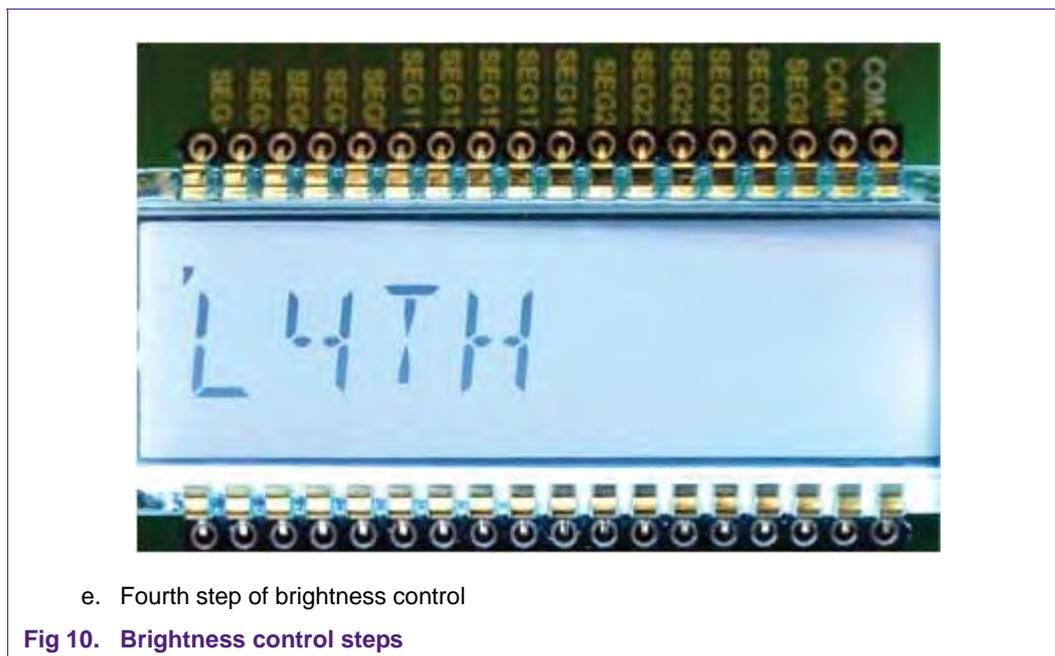

4. Charge pump

If only a low supply voltage is available but the display needs a higher value, a simple charge pump can be implemented by using the CLK output.


4.1 Basic set-up

[Figure 11](#) depicts the basic set-up. If diodes D1 and D2 have a threshold voltage of V_{th} , the generated V_{LCD} calculates to

$$V_{LCD} = 2 \times (V_{DD} - V_{th}) - V_{DO} \quad (2)$$


with V_{DO} as the drop-out voltage across the equivalent resistor formed by the charge pump. This seems to be sufficient to drive a 5 V display from a Lithium battery.

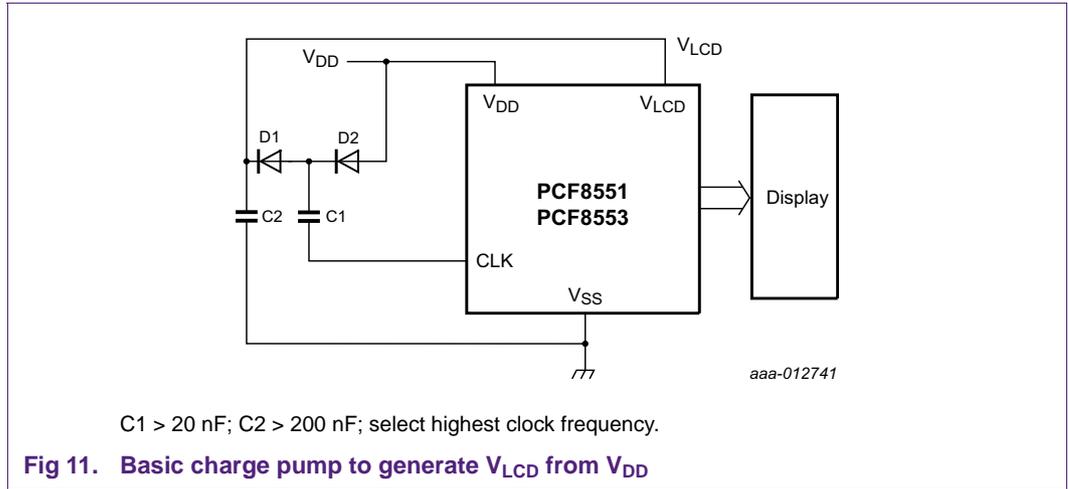While silicon diodes exhibit a threshold of ~ 0.6 V, the drop across D1/D2 can be reduced by using Schottky diodes with a threshold of ~ 0.3 V.



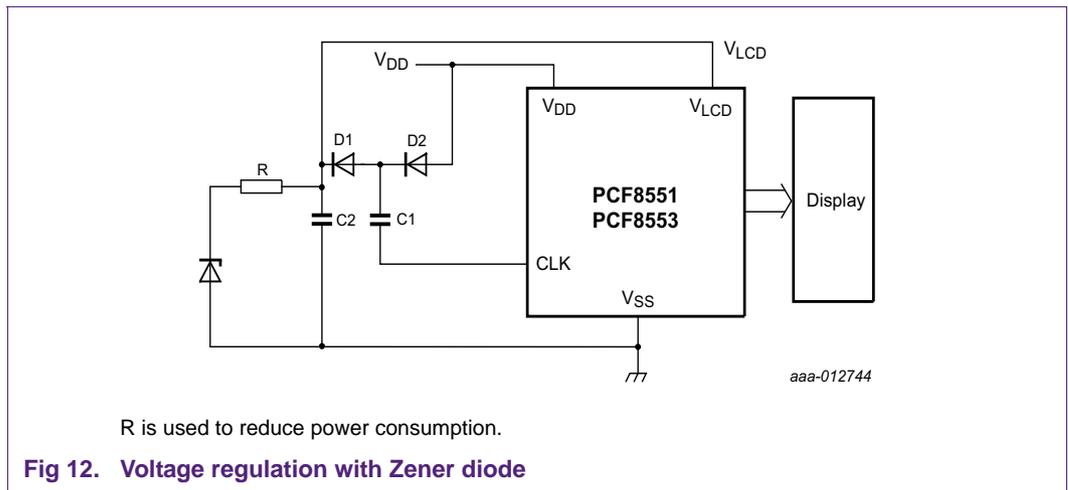4.2 Simple voltage regulation

In principle, the charge pump is unregulated, but to prevent overvoltage a certain amount of control may be required. One possibility could be using an LDO for this task. But the requirements on the LDO are probably difficult to fulfill with a standard catalog element. So the simpler variant with a Zener diode will probably be a more reasonable solution (see [Figure 12](#)).



4.3 Voltage ripple

Voltage ripple is determined by f_{CLK} , I_{load} and can be controlled with the size of C2.

$$V_{ripple} = \frac{I_{load}}{f_{CLK} \times C2} \tag{3}$$

5. Power-on reset

Chip variants, which comprise an $\overline{\text{RST}}$ pin can be reset at power-on by adding a capacitor on this pin. The value of this capacitor depends on the rising slope of V_{DD} .

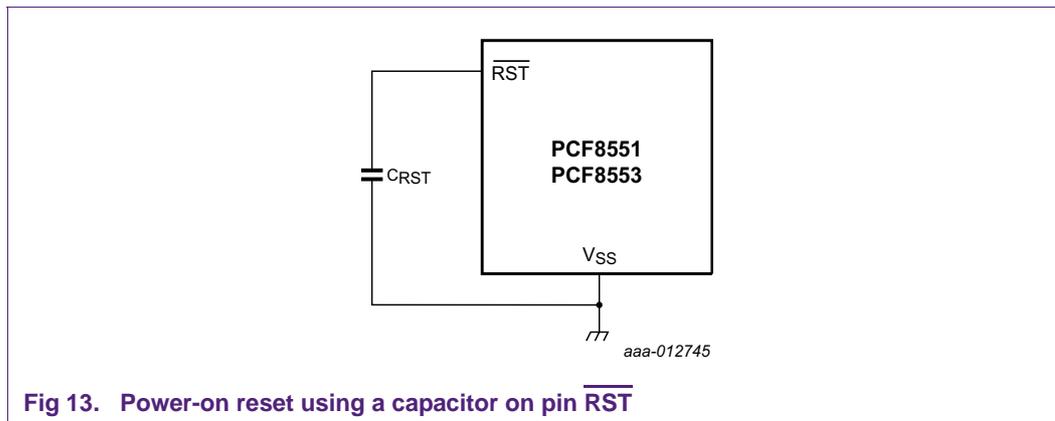


Fig 13. Power-on reset using a capacitor on pin $\overline{\text{RST}}$

5.1 Power-on with a slowly starting power supply

The built-in POR block acts on the rising edge of the V_{DD} supply voltage. It is designed to react to fast slopes. If the system supply starts slowly, it is recommended to initiate a software reset immediately after power-on.

6. References

- [1] PCF8551 — Data sheet
- [2] PCF8553 — Data sheet
- [3] DE-301-RGB/A — Display Elektronik GmbH, 24-January-2011

7. Legal information

7.1 Definitions

Draft — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

7.2 Disclaimers

Limited warranty and liability — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. NXP Semiconductors takes no responsibility for the content in this document if provided by an information source outside of NXP Semiconductors.

In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the *Terms and conditions of commercial sale* of NXP Semiconductors.

Right to make changes — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors and its suppliers accept no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

Applications — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product

design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

Export control — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

Evaluation products — This product is provided on an "as is" and "with all faults" basis for evaluation purposes only. NXP Semiconductors, its affiliates and their suppliers expressly disclaim all warranties, whether express, implied or statutory, including but not limited to the implied warranties of non-infringement, merchantability and fitness for a particular purpose. The entire risk as to the quality, or arising out of the use or performance, of this product remains with customer.

In no event shall NXP Semiconductors, its affiliates or their suppliers be liable to customer for any special, indirect, consequential, punitive or incidental damages (including without limitation damages for loss of business, business interruption, loss of use, loss of data or information, and the like) arising out of the use of or inability to use the product, whether or not based on tort (including negligence), strict liability, breach of contract, breach of warranty or any other theory, even if advised of the possibility of such damages.

Notwithstanding any damages that customer might incur for any reason whatsoever (including without limitation, all damages referenced above and all direct or general damages), the entire liability of NXP Semiconductors, its affiliates and their suppliers and customer's exclusive remedy for all of the foregoing shall be limited to actual damages incurred by customer based on reasonable reliance up to the greater of the amount actually paid by customer for the product or five dollars (US\$5.00). The foregoing limitations, exclusions and disclaimers shall apply to the maximum extent permitted by applicable law, even if any remedy fails of its essential purpose.

Translations — A non-English (translated) version of a document is for reference only. The English version shall prevail in case of any discrepancy between the translated and English versions.

7.3 Trademarks

Notice: All referenced brands, product names, service names and trademarks are the property of their respective owners.

8. Figures

Fig 1.	Relation of frame frequency (f_{fr}), clock frequency (f_{clk}) and multiplex-rate (n_{MUX})	3
Fig 2.	Speaker/buzzer set-up	4
Fig 3.	Basic backlight set-up	5
Fig 4.	Set-up with brightness control	5
Fig 5.	Driving more than one LED	6
Fig 6.	Potential temperature compensation	6
Fig 7.	Set-up with multi-color brightness control	7
Fig 8.	Schematic of the use case	7
Fig 9.	Waveforms of SEGn output controlling N-channel gate	10
Fig 10.	Brightness control steps	13
Fig 11.	Basic charge pump to generate V_{LCD} from V_{DD}	14
Fig 12.	Voltage regulation with Zener diode	14
Fig 13.	Power-on reset using a capacitor on pin RST	15

9. Contents

1	Introduction	3
2	Buzzer	3
3	Backlight control	5
3.1	Basic solution	5
3.2	Solution with brightness control	5
3.3	Multi-color with brightness control	7
3.4	Case of application	7
3.4.1	Schematic and elements	7
4	Charge pump	13
4.1	Basic set-up	13
4.2	Simple voltage regulation	14
4.3	Voltage ripple	14
5	Power-on reset	15
5.1	Power-on with a slowly starting power supply	15
6	References	15
7	Legal information	16
7.1	Definitions	16
7.2	Disclaimers	16
7.3	Trademarks	16
8	Figures	17
9	Contents	18

Please be aware that important notices concerning this document and the product(s) described herein, have been included in section 'Legal information'.

© NXP Semiconductors N.V. 2014.

All rights reserved.

For more information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: salesaddresses@nxp.com

Date of release: 27 June 2014

Document identifier: AN11566