



Copy 27C64 to 28C64, controlled by Arduino UNO

(for 27/28C128 add A13)

Reading and writing through Arduino is also available

A01234

00111 start

set addr low and A12 to A5 here

10111 addr low in, rising edge of A0

set addr high and alt A13 to A5 here

11111 addr high in, rising edge of A1

11110 addr out

11100 27C64 data read

wait, notify D7

01000 28C64 write addr, falling edge

11000 28C64 write data, rising edge

11010 disable 27C64

10010 28C64 data read

or wait the whole thing out

D7 is inverted until writing is done

10111 disable address and 28C64

00111 next address

3rd LS374 is also possible, it can be clocked with A2, but then A0, A1 and A2 must be pulsed down, only one control down does not activate EEPROM, but multiple socket sizes may need their own control chip

PROM programming is also possible,
then A0 and A1 can be used for control